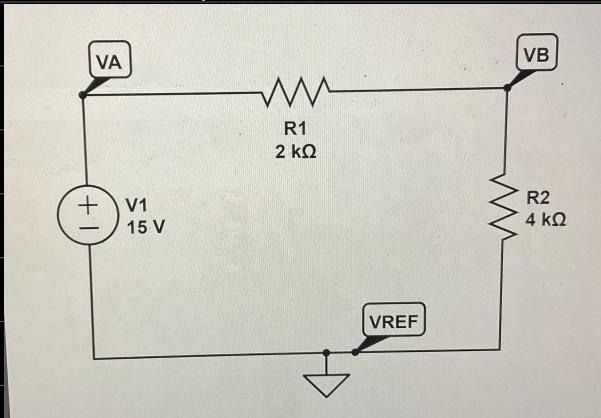


Homework 1

(1) The circuit



The values:

V(VA)	15.00 V
V(VB)	10.00 V
V(VREF)	0.000 V
V(VA)-V(VB)	5.000 V
P(V1)	-37.50 mW
P(R1)	12.50 mW
P(R2)	25.00 mW

My Calculations


(a) $P_{V_1} = V_1 = 15V \times 2.5mA = -37.50mW$

(b) $P_{R_1} = I^2 R = 2.5^2 \times 2000 = 12.5mW$

(c) $P_{R_2} = I^2 R = 2.5^2 \times 4000 = 25.0mW$

∴ No Discrepancies

(2) The plot:

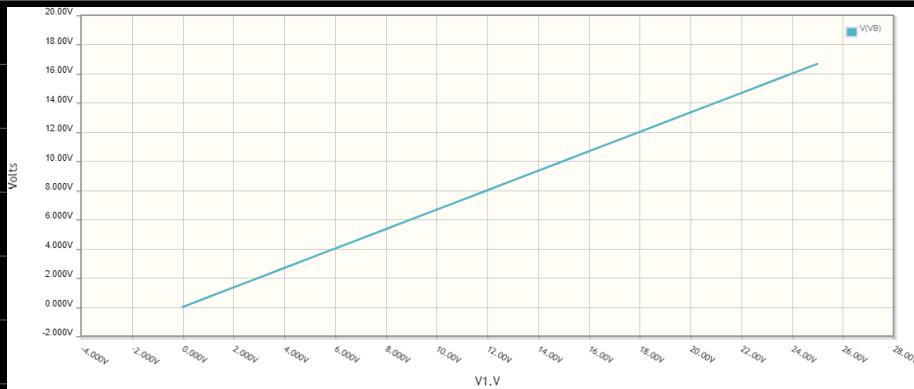


Recorded Voltage is 18.5 ± 2 mV

My Calculations:


$$\text{Voltage divider} = V \times \frac{R_2}{R_1 + R_2} \Rightarrow 25 \times \frac{\frac{4}{6}}{\frac{2}{6}} = \frac{50}{3} = 16.67mV$$

∴ My value is smaller. I don't know why. I probably did not get the calculation right.

(b) The plot:

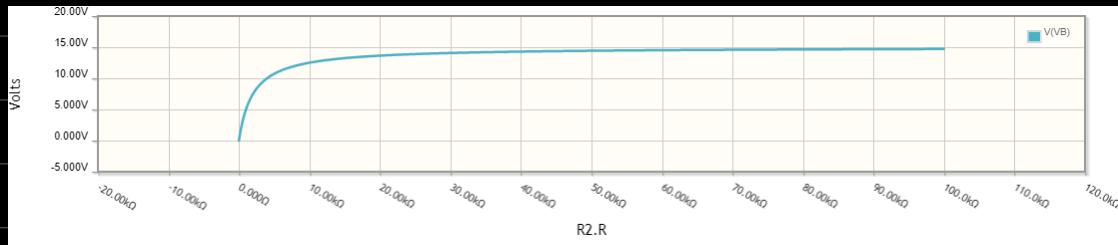


The plot for the power.

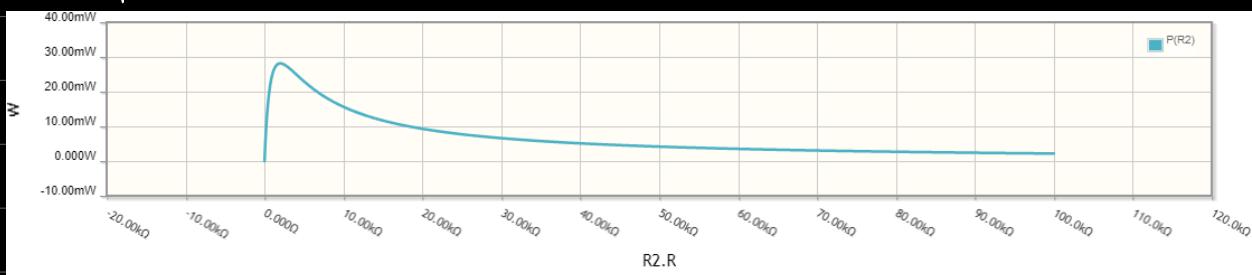

Recorded values: $R_2 = 1.700\text{k}\Omega$, Power = 27.94 mW

The value of R_2 is smaller than R_1 .

(d) The plot:

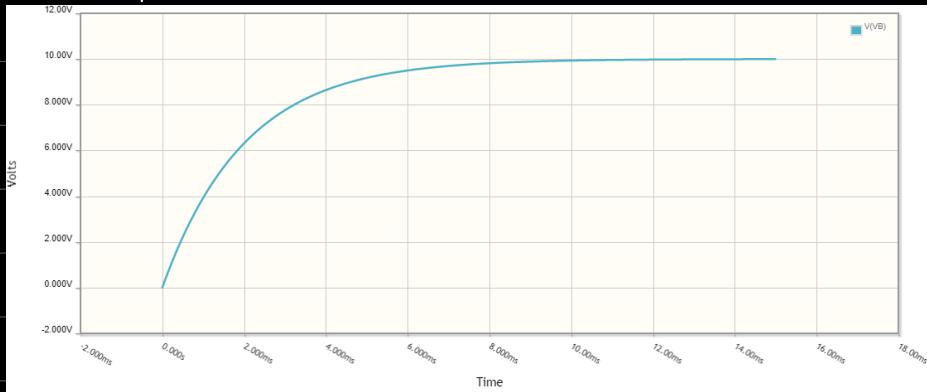


$$T = RC = 2 \times 10^3 \times 1 \times 10^{-6} = 2 \times 10^{-3}$$


$$5T = 0.005\text{ms}$$

~

(5) The circuit

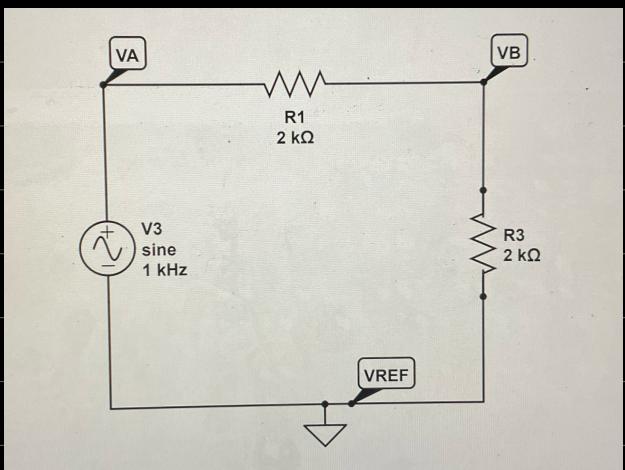

The plot:

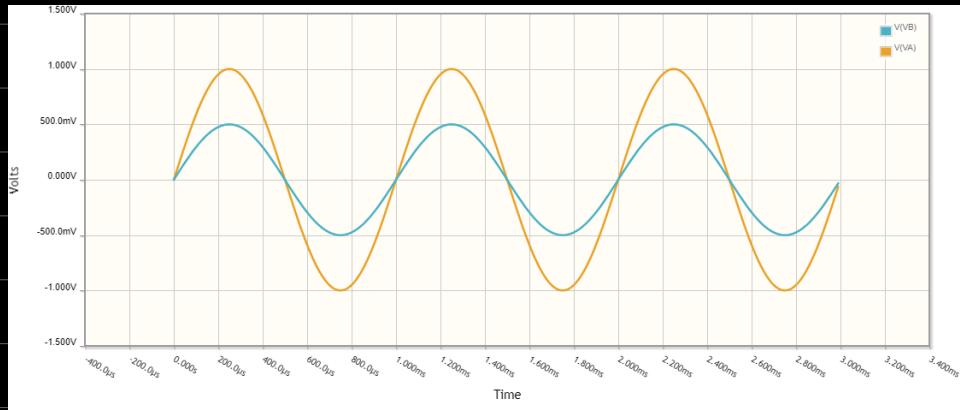

Peak voltage of $V_A = 1.000V$

Peak voltage of $V_B = 500.0mV$

The phase relationship is 0 rad because they are on the same frequency.