

1) Calculating α and β relationships


Knowing that $\alpha = \frac{\beta}{1+\beta}$ and $\beta = \frac{\alpha}{1-\alpha}$, fill in the following tables with the missing parameters.

Calculate α to four decimal places. (a spreadsheet app, such as Microsoft Excel, could be helpful)

| | | | | | |
|------------|------|------|-------|-------|-------|
| $\alpha =$ | 0.98 | 0.99 | 0.995 | 0.996 | 0.998 |
| $\beta =$ | | | | | |

| | | | | | | |
|------------|----|----|-----|-----|-----|-----|
| $\beta =$ | 50 | 75 | 100 | 150 | 200 | 300 |
| $\alpha =$ | | | | | | |

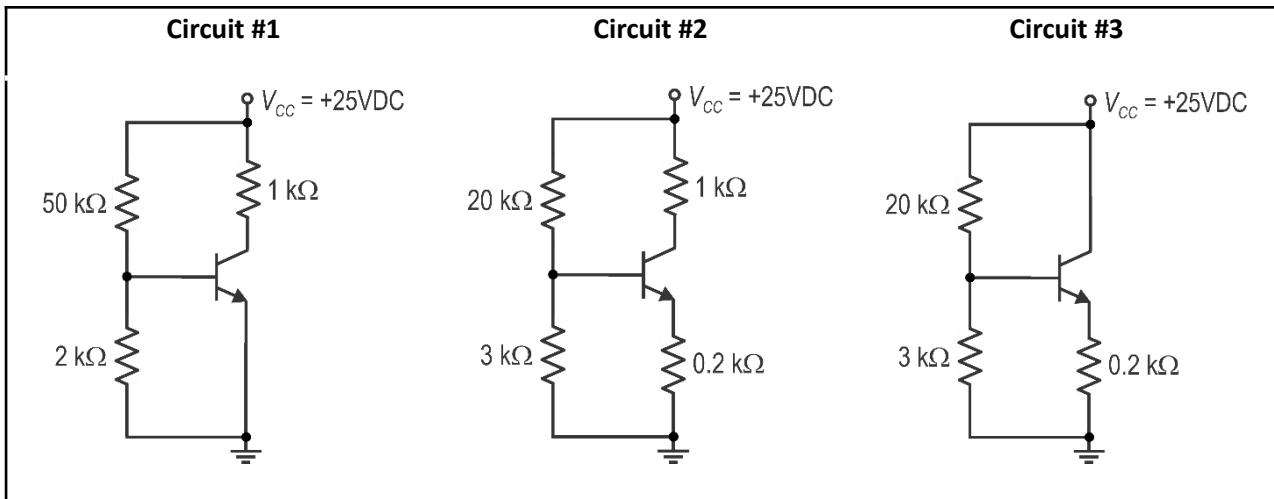- 2) **BJT DC Parameters:** For the following three BJT circuits operating at DC, **and referring to Example 6.10 in the textbook**, calculate the associated parameters. Use $\beta = 100$, $V_{BE,ON} = 0.7$ V and $V_{CE,SAT} = 0.3$ V.



- a) Calculate I_{BQ} , I_{CQ} and V_{CEQ} for each of the three circuits above. Also state if $V_{CEQ} > V_{CEQ,SAT}$.

| | Circuit #1 | Circuit #2 | Circuit #3 |
|-----------|------------|------------|------------|
| I_{BQ} | | | |
| I_{CQ} | | | |
| V_{CEQ} | | | |

| | | | |
|---------------------|--|--|--|
| $V_{CEQ} > V_{CEO}$ | | | |
| SAT | | | |


- b) For each of these three circuits, calculate the percent change in I_{CQ} when β is changed from 100 to 150
? Place your results in a table.

$$\% \text{ Change in } I_{CQ} = \left(\frac{I_{CQ,100} - I_{CQ,150}}{I_{CQ,100}} \right) \times 100\%$$

| | Circuit #1 | Circuit #2 | Circuit #3 |
|----------------------|------------|------------|------------|
| % Change in I_{CQ} | | | |

3) BJT circuit at DC:

Use $V_{BE,ON} = 0.7 \text{ V}$

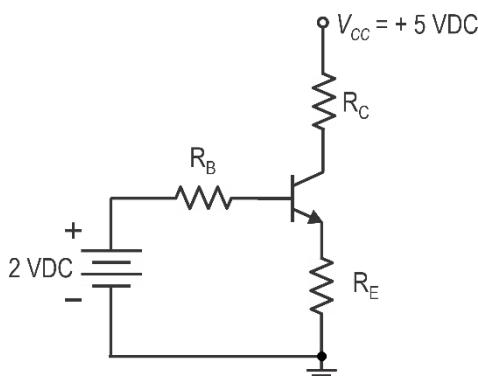

- a) For $I_{CQ} = 0.8 \text{ mA}$ and $V_{CEO} = 2 \text{ V}$, find R_C and R_B using $R_E = 0$, $\beta = 80$
- b) For $I_{CQ} = 0.8 \text{ mA}$ and $V_{CEO} = 2 \text{ V}$, find R_C and R_B using $R_E = 1 \text{ k}\Omega$, $\beta = 80$
- c) Using the resistor values found in (a), change $\beta = 120$ and calculate the new I_{CQ} and V_{CEO}
- d) Using the resistor values found in (b), change $\beta = 120$ and calculate the new I_{CQ} and V_{CEO}
- e) Which design, (a) or (b), makes I_{CQ} less sensitive to changes in β ? Briefly discuss how you reached that conclusion (in words, a calculation, a table, or other).


| | A | B |
|---|-------|------|
| 1 | Alpha | Beta |
| 2 | 0.98 | 49 |
| 3 | 0.99 | 99 |
| 4 | 0.995 | 199 |
| 5 | 0.996 | 249 |
| 6 | 0.998 | 499 |

file. Save

| | | |
|----|------|------------------|
| 9 | Beta | Alpha |
| 10 | | |
| 11 | | 50 0.9803921569 |
| 12 | | 75 0.9868421053 |
| 13 | | 100 0.9900990099 |
| 14 | | 150 0.9933774834 |
| 15 | | 200 0.9950248756 |
| 16 | | 300 0.9966777409 |

Close < > Sheet1 +


(2)
(1)

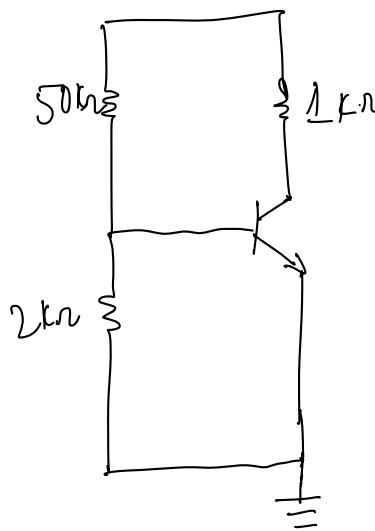

$$V_{cc} = 25V$$

$$V_{Th} = 25 \times \frac{2}{52} = 0.9615V$$
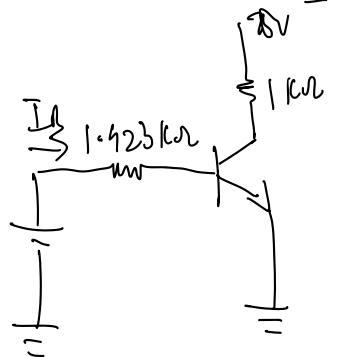
$$R_{Th} = \frac{50 \times 2}{52} = 1.923k\Omega$$



$$(I_B)_Q = \frac{0.9615 - 0.7}{1.923} = 0.136mA$$

$$(I_C)_Q = 100 \times 0.136 = 13.6mA$$

$$(V_{CE})_Q = 25 - (1 \times 13.6) = 11.4V$$

If $f = 20$:

$$(I_C)_Q = 200 \times 0.136 = 27.2mA$$


$$(V_{CE})_Q = 25 - 27.2 = -2.2V$$

$(V_{CE})_Q < (V_{CE})_{sat}$ So the transistor is in saturation mode

$$(I_C)_Q \neq 27.2mA$$

$$(I_C)_Q = \frac{25 - 0.3}{1k\Omega} = 24.3mA$$

(ii)

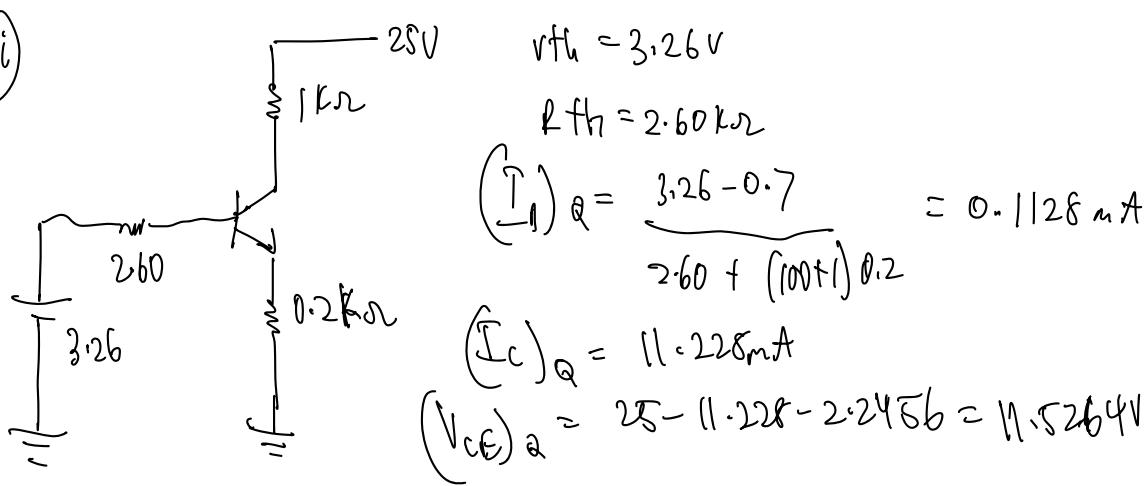If $\beta = 200$:


$$(\bar{I}_C)_Q = 22.456mA$$

$$(\bar{V}_{CE})_Q = 25 - 22.456 - 4.4912 = -1.9472$$

$$(\bar{V}_{CE})_Q < (\bar{V}_{CE})_{sat}$$

$$\therefore (\bar{I}_C)_Q = \frac{25 - 0.3}{1.2} = 20.5633mA$$

(iii)

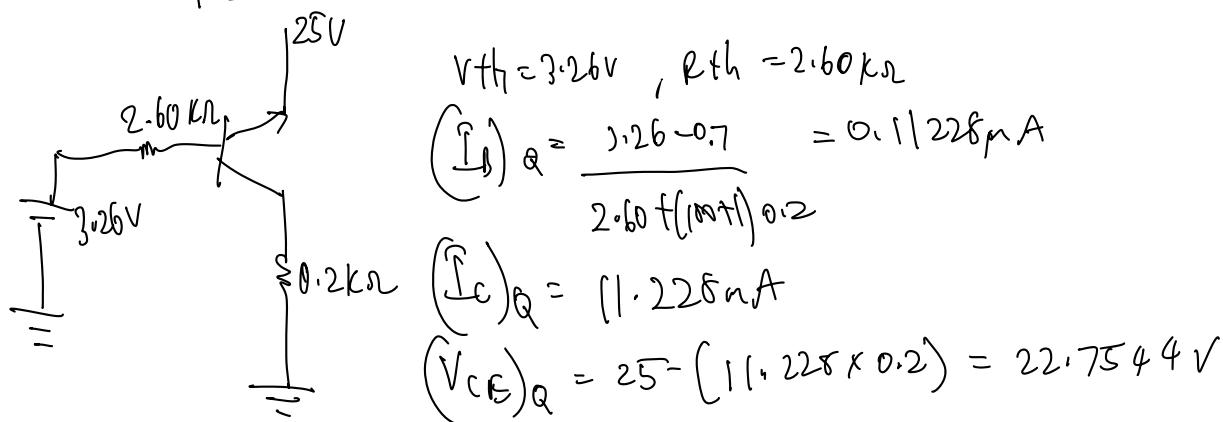If $\beta = 200$:

$$(\bar{I}_C)_Q = 22.456mA$$

$$(\bar{V}_{CE})_Q = 25 - (22.456 \times 0.2) = 20.508$$

$$(\bar{V}_{CE})_Q > (\bar{V}_{CE})_{sat} \quad \text{Device is in active mode}$$

$$\therefore (\bar{I}_C)_Q = 22.456mA$$

| | Circuit #1 | Circuit #2 | Circuit #3 |
|---------------------------|------------|------------|------------|
| I_{BQ} | 0.136 mA | 0.11228 mA | 0.11228 mA |
| I_{CQ} | 13.6 mA | 11.228 mA | 11.228 mA |
| V_{CEQ} | 11.4 V | 11.526 V | 22.754 V |
| $V_{CEQ} > V_{CEQ_{SAT}}$ | Yes | Yes | Yes |

(b)

| | Circuit #1 | Circuit #2 | Circuit #3 |
|----------------------|------------|------------|------------|
| % Change in I_{CQ} | -81.6% | -83.32% | -100% |

(b) (i) $I_{CQ} = 0.1 \text{ mA}, V_{CEQ} = 2V, \beta = 80, R_E = 0$

$$-V_C + I_{CQ}(R_C) + V_{CEQ} = 0$$

$$-5 + (0.1 \times 10^{-3}) R_C + 2 = 0$$

$$R_C = \frac{5-2}{0.8 \times 10^{-3}} = 3.75 \text{ k}\Omega$$

LVL at i/p:

$$-2 + I_B R_S + I_E R_E = 0 \quad \beta = \frac{I_{CQ}}{I_{BQ}}$$

$$-2 + I_B R_S = 0 \quad I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.1 \text{ mA}}{80} = 1.25 \text{ mA}$$

$$R_S = \frac{2}{1.25 \text{ mA}} = 1.6 \text{ k}\Omega$$

(b) (ii) $I_{CQ} = 0.8 \text{ mA}, V_{CEQ} = 2V, \beta = 80, R_E = 1k$

$$-V_C + I_{CQ}(R_C) + V_{CEQ} + I_E R_E = 0$$

$$-5 + I_{CQ}(R_C + R_E) + 2 = 0$$

$$I_{CQ}(R_C + R_E) = 3$$

$$R_C + R_E = \frac{3}{0.8 \text{ mA}} = 3.75 \text{ k}\Omega$$

$$R_C = 3.75 - 1k = 2.75 \text{ k}\Omega$$

KVL at i/p:

$$-2 + I_B R_B + I_E R_E = 0$$

$$-2 + I_B R_B + \beta (I_B) R_E = 0$$

$$-2 + I_B (R_B + \beta R_E (\beta + 1)) = 0$$

$$I_B (R_B + 81 \times 10^3) = 2$$

$$R_B + 81K = \underline{2}$$

$$10\mu A$$

$$I_E = I_C + I_B$$

$$= \beta I_B + I_B = I_B (\beta + 1)$$

$$R_B = \frac{2}{10\mu A} - 81K = 1.9M\Omega$$

(C) KVL at i/p:

$$-2 + I_B R_B + I_E R_E = 0$$

$$I_B R_B = 2$$

$$I_B = \frac{2}{R_B} = \frac{2}{200K} = 10\mu A$$

$$I_C = \beta I_B = 120 (10\mu A) = 1200\mu A$$

KVL at output:

$$-5 + 1200 \times 10^{-6} (3.75) + V_{CEQ} = 0$$

$$V_{CEQ} = 5 - 1200 (3.75) \times 10^{-3} = 0.05V$$

(d)

KVL at i/p:

$$-2 + I_B R_B + I_E R_E = 0$$

$$-2 + I_B R_B + \beta I_E R_E (\beta + 1) = 0$$

$$I_B (R_B + \beta R_E (\beta + 1)) = 2$$

$$I_B = \frac{2}{1.91 \times 10^6 + 12K} = 0.98\mu A$$

$$I_E = I_C + I_B$$

$$= \beta I_B + I_B = I_B (\beta + 1)$$

$$I_C = \beta I_B = 120 \times 0.98\mu A = 117.6\mu A$$

MVL at 8/8 :

$$-5 + 117.6 \times 10^{-6} (2.75k) + V_{CEQ} + I_E(1k) = 0$$

$$-5 + 117.6 \times 10^{-6} (2.75) + V_{CEQ} + I_E(1k)(\beta+1) = 0$$

$$-5 + 117.6 \times 10^{-6} (2.75k) + V_{CEQ} + (121)(0.98 \times 10^{-6}) (1k) = 0$$

$$V_{CEQ} = 5 - 117.6 \times 10^{-6} (2.75k) - (121 \times 0.98 \times 10^{-6} (1k)) = 4.55V$$