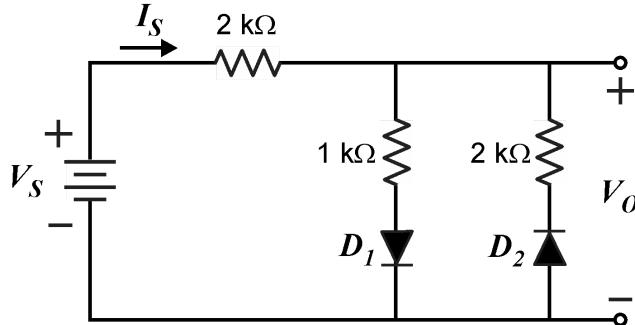


- 1) **Diode Transfer Characteristics:** if V_S is varied over the range $-3V \leq V_S \leq +3V$, plot the transfer characteristic for V_O (y-axis) versus V_S (x-axis). Hand drawn plots are acceptable.

When the diode is ON, use the “constant-voltage drop model” with $V_{D,ON} = 0.7$ V.




- 2) **Diode Transfer Characteristics:** Using a PSpice simulator, such as CircuitLab, simulate the transfer characteristics for V_O (y-axis) versus V_S (x-axis) using the circuit in Problem #1. Simulate a DC sweep with V_S varied over the range $-3V \leq V_S \leq +3V$. The PSpice diode can be the 1N4148 or equivalent. Submit your PSpice schematic and the simulated plot of the transfer characteristics. Comment on your hand calculated solutions in comparison to the simulated
- 3) **Diode Transfer Characteristics:** if I_{IN} is varied over the range $0 \leq I_{IN} \leq 2mA$, plot the transfer characteristic for the following (hand drawn plots are acceptable).

When the diode is ON, use the “constant-voltage drop model” with $V_{D,ON} = 0.7$ V.

a. V_O (y-axis) versus I_{IN} (x-axis)


b. I_D (y-axis) versus I_{IN} (x-axis).

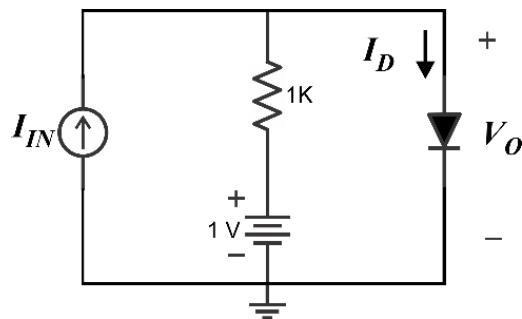


- 4) **Diode/Zener Transfer Characteristics:** if V_{IN} is varied over the range $-10 \leq V_{IN} \leq +10V$, plot the transfer characteristic for the following (hand drawn plots are acceptable). When the diode is ON (forward biased region), use the “constant-voltage drop model” with $V_{D,ON} = 0.7$ V. Diodes D1, D2 and D3 are all the same type. Diode D4 is a Zener with $V_Z = 3V$.

a. V_O (y-axis) versus V_{IN} (x-axis)

b. I_o (y-axis) versus V_{IN} (x-axis)

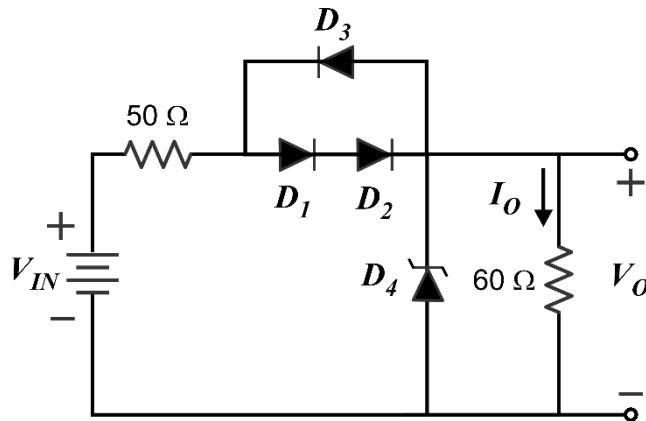

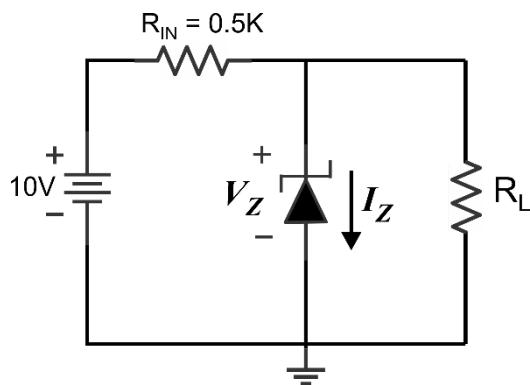- 5) **Zener Diode Analysis:** Knowing that the Zener was selected for a breakdown of $V_z = +6.8V$, answer the following questions. Also note that the Zener is rated for a maximum power dissipation of 500 mW ($P_{z, MAX} = 500 \text{ mW}$).
- Determine I_z with $R_L = \infty$
 - Calculate the power dissipation, P_z in the Zener diode with $R_L = \infty$. Does this value exceed the specified maximum power dissipation for the Zener?
 - Find R_L such that I_z is 10% of the value of I_z found in (a).
 - If $R_L = 0.1 \text{ k}\Omega$, what is the minimum value for R_{IN} such that the Zener diode does not exceed the rated power dissipation of 500 mW ($P_{z, MAX}$)?



Solutions:

① D₁ will be on when V_s > 0.7V

$$0.7 < V_s < 3$$

$$I_S = \frac{V_S - 0.7}{2+1} \text{ mA} = \frac{V_S - 0.7}{3} \text{ mA}$$

$$V_O = 0.7 + I_S \times 1 = 0.7 + \frac{V_S - 0.7}{3}$$

when, $-3 < V_S < 0.7$

$$I_S = -\frac{V_S + 0.7}{4} \text{ mA}$$


$$V_O = -(0.7 + 2 \times I_S) = -(0.7 + 2 \times \frac{V_S + 0.7}{4}) \text{ V}$$

When $-0.7 < V_S < 0.7$


D₁ and D₂ will be off

Hence

$$V_O = V_S$$

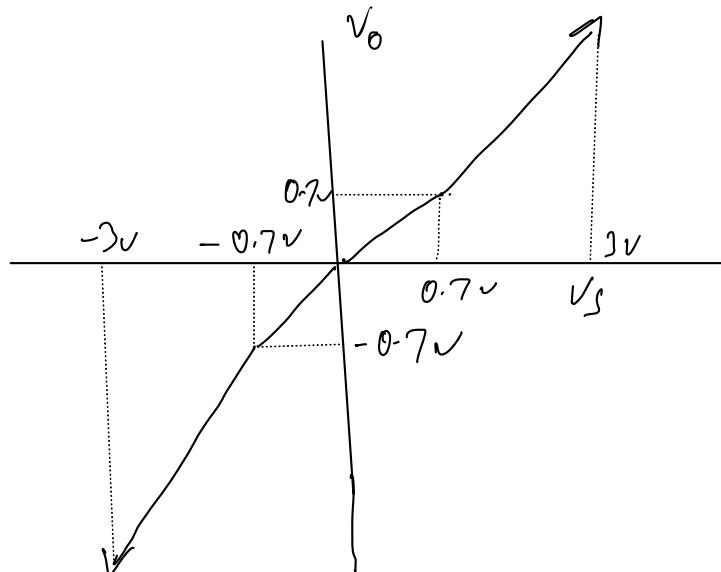

②

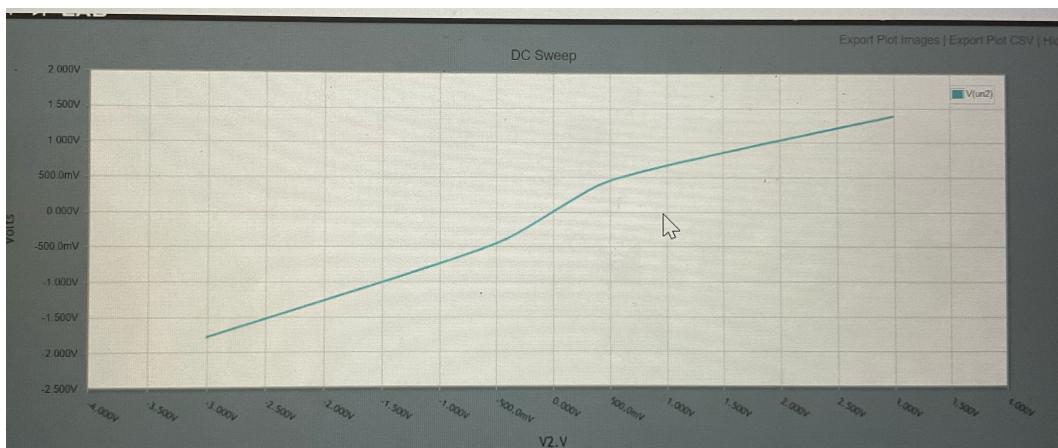


They are the same as my calculations

$$\textcircled{3} \quad 0 \leq I_{in} \leq 2 \text{ mA}$$

$$V_o = 0.7 \text{ V}$$

$$\frac{V_o - 1}{1\text{K}} + I_D = I_{in}$$
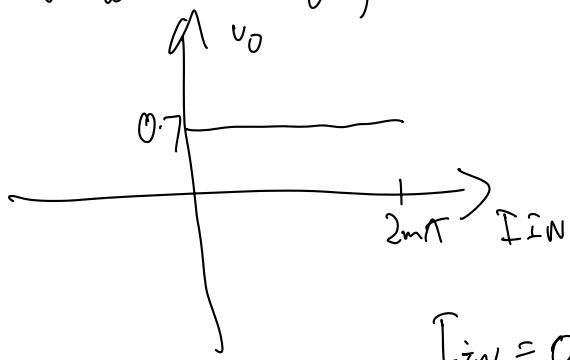
$$\textcircled{4} \quad V_o(y) \text{ vs } I_{in}(x)$$



$$I_{in} = 0$$

$$\frac{V_o - 1}{1\text{K}} + I_D = 0$$

$$V_o - 1 = -I_D(1\text{K})$$

$$V_o = -I_D(1\text{K}) + 1$$

$$I_{in} = 1$$

$$V_o - 1 + I_D = 1\text{K}$$

$$V_D - 1 = 1\text{K} - I_D(1\text{K})$$

$$V_D = 1\text{K} - I_D(1\text{K}) + 1$$


$$V_D \Rightarrow (1 - I_D)1\text{K} + 1$$

depends on I_D

diode is off $V_D \approx 0$, $I_D = 0$

diode is on $V_D = 0.7$, $V_o = 0.7$

\textcircled{5}

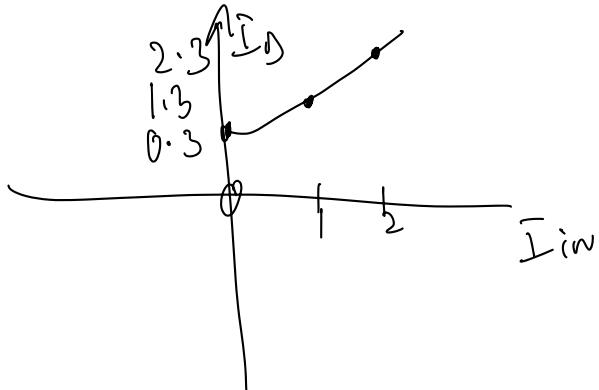

$$\frac{V_D - 1}{1\text{K}} + I_D = I_{in}$$

when diode is on

$$\frac{0.7 - 1}{1\text{K}} + I_D = I_{in}$$

$$I_{in} = 0, I_D = 0.3 \text{ mA}$$

$$I_{in} = 1 \text{ mA}, I_D = 1.3 \text{ mA}$$

$$I_{in} = 2 \text{ mA}, I_D = 2.3 \text{ mA}$$


When diode is off

$$\frac{0-1}{1k} + I_D = I_{in} \quad (I_D = 0)$$

$$(4) \quad 0 \leq V_{in} \leq 1.4 \text{ V}$$

D_1, D_2 forward bias but blocking mode $V_o = 0V$

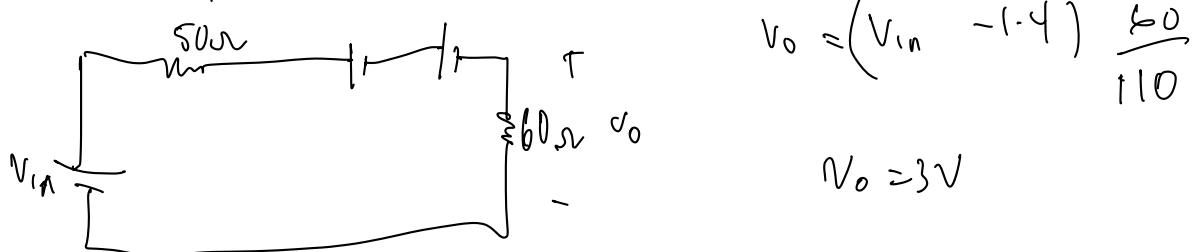$1.4V < V_{14} < 3V$ D_1 and D_2 forward conduction mode



$$3V = (V_{in} - 1.4) \frac{60}{110} \Rightarrow V_{in} = 6.9V$$

$$\therefore 0 < V_{in} < 1.4V \Rightarrow V_o = 0$$

$$1.4 < V_{in} < 6.9V \Rightarrow 0 < V_o < 3V$$


$$6.9V < V_{14} \quad V_o = 3V$$

$$\left. \begin{array}{l} I = 0 \\ 0 < I_o < 50 \text{ mA} \\ I_o = 50 \text{ mA} \end{array} \right\}$$

During ($0 \leq V_{in} < 1.4V$)

$$0 \text{ to } -0.7V$$

$$-0.7 \text{ to } -1.4V$$

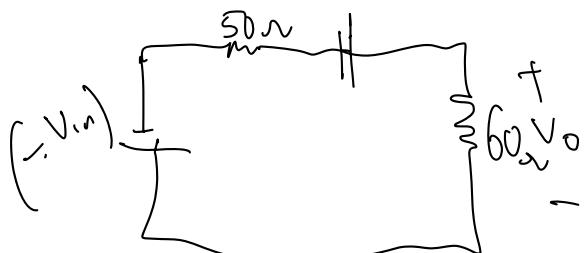

$$V_o = \underbrace{-V_{in} + 0.7}_{110} \times 60$$

When $V_0 = -0.7$

$$-0.7 = \underbrace{-V_{in} + 0.7}_{110} \times 60$$

$$V_{in} = -1.9833$$

V_{in}

$$0 \text{ to } -0.7 \Rightarrow V = 0$$

$$0.7 \text{ to } -1.9833 \quad V = 0 \text{ to } 0.7V$$


$$0.7 \text{ to } -10 \quad V = -0.7V$$

$$I_o = 0$$

$$I_o \approx 0 \text{ to } -1.166 \text{ mA}$$

$$I_o = -1.166 \text{ mA}$$

$$I_o = \frac{V_0}{60}$$

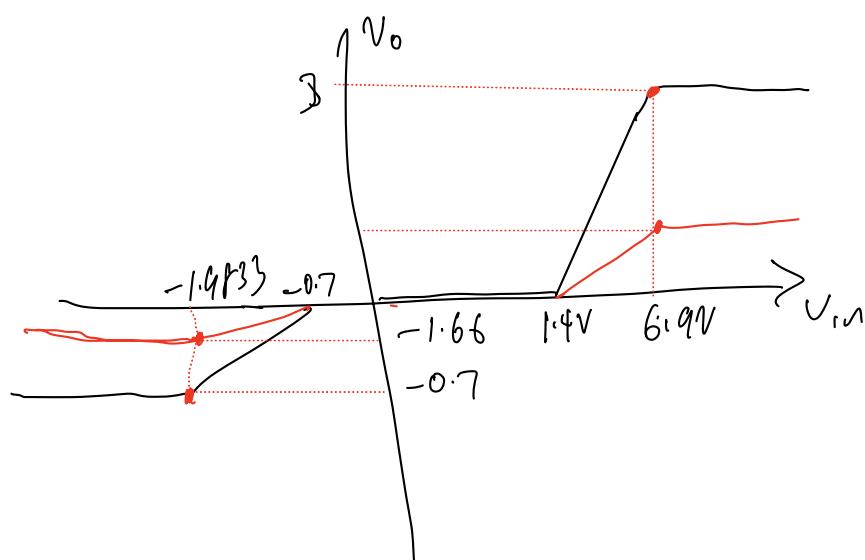


(5)

$$V_2 = 6.8V$$

$$P_{2\max} = 50 \text{ mW}$$

(6) $R_L = \text{infinite}$

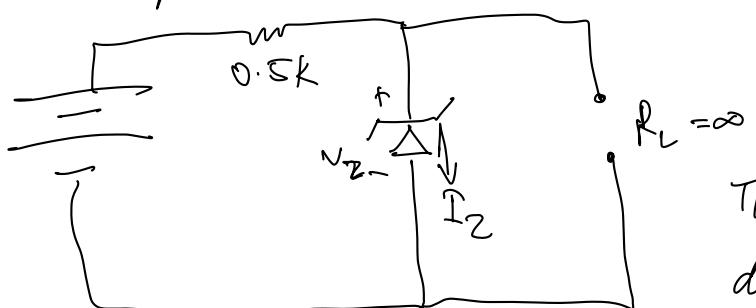

$$I_2 = \frac{10 - V_2}{0.5k}$$

The zener diode will break down

$$I_2 = \frac{10 - 6.8}{0.5k} = 6.4 \text{ mA}$$

$$\textcircled{b} \quad P_2 = V_2 I_2 = 6.8 \times 6.4 \times 10^{-3} = 43.52 \text{ mW} \quad \text{and} \quad I_{2\max} = 50 \text{ mW}$$

\therefore Not exceeding the specified power dissipation

$$\textcircled{c} \quad I_2 = 6.4 \times 10^{-3} \times \frac{10}{100} = 0.64 \text{ mA}$$

$$I = \underbrace{6.8}_{R_U} + 0.64 \times 10^{-3}$$

Now,

$$\begin{aligned} & (10 - I(0.5 \times 10^3)) \approx 6.8 \\ & = \left(\underbrace{6.8}_{R_U} + 0.64 \times 10^{-3} \right) \left(0.5 \times 10^3 \right) \approx 3.2 \\ & = \frac{3.2 \times 10^3}{R_L} = 0.32 = 3.2 \end{aligned}$$

$$\approx R_U = 1.18 \text{ k}\Omega$$

$$\textcircled{d} \quad V_2 I_2 < 500 \text{ mW}$$

$$I_2 < \frac{500}{6.8} \text{ mA}$$

$$I_2 < 73.52 \text{ mA}$$

$$I_2 = \underbrace{6.8}_{R_U} = \frac{6.8}{0.1} \text{ mA} = 68 \text{ mA}$$

$$\Rightarrow \underbrace{10 - 6.8}_{R_{in}} < (I_2 + I_U)$$

$$= \frac{3.2}{R_{in}} < (73.52 + 0.1) \text{ mA}$$

$$= R_{in} > \frac{3.2}{141.62} \text{ mA}$$

$$> R_{in} > 22.61 \text{ }\Omega$$