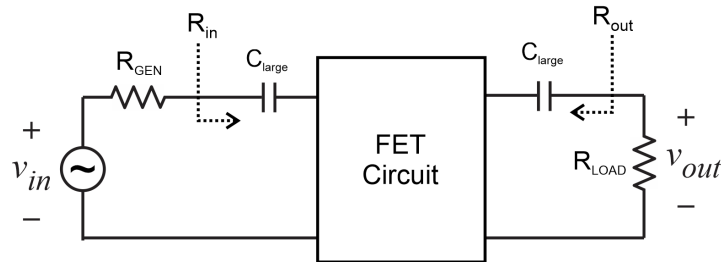


- 1) **Small Signal Parameters:** For the following FET amplifiers, you are going to obtain the small signal parameters,  $A_V$  (voltage gain),  $R_{in}$  and  $R_{out}$  using the circuits from homework assignment #3. The circuits from assignment #4 fit into the box shown here. The sinusoidal generator,  $v_{in}$ , has an internal resistance  $R_{GEN}$ . The amplifier output drives a resistive load,  $R_{LOAD}$ .



The FET parameters are  $V_{TN} = 2.6V$ ,  $k_N = 0.12 A/V^2$ ,  $V_A = \text{large}$ . For each circuit, the bias point (Q-point) is the same as found in homework assignment #5 with  $V_{GS} = 3.0 V$ ,  $I_{DQ} = 9.6 mA$  and  $V_{DS} = 10.4 V$ . For this assignment you do not need to repeat the calculations of the DC parameters (Step 1). In this case, the FET is “saturated” and we will assume that the FET is operating under the small signal condition having a magnitude of  $v_{in}$  that places  $v_{gs} \ll k_n(V_{GS} - V_{TN})$  (requirement for small signal).


For the following circuits, use a generator resistance and load resistance of




$$R_{GEN} = 1 \text{ k}\Omega$$

$$R_{LOAD} = 1 \text{ k}\Omega$$

Find  $A_V$  (voltage gain),  $R_{in}$  and  $R_{out}$  for each of the following circuits (A-D).

A) Common Source Amplifier

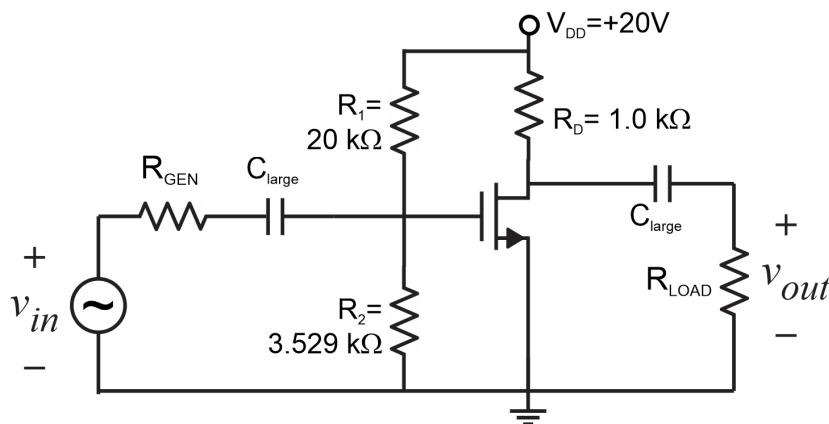

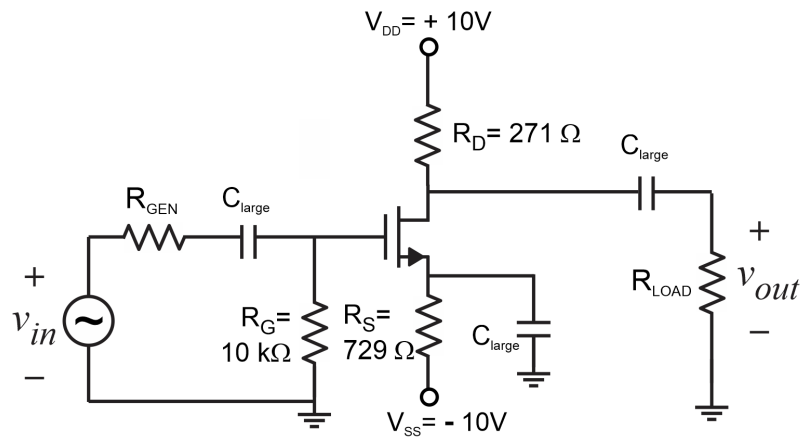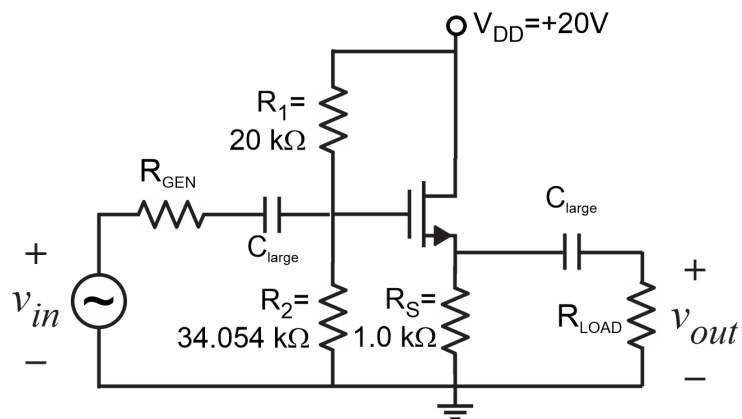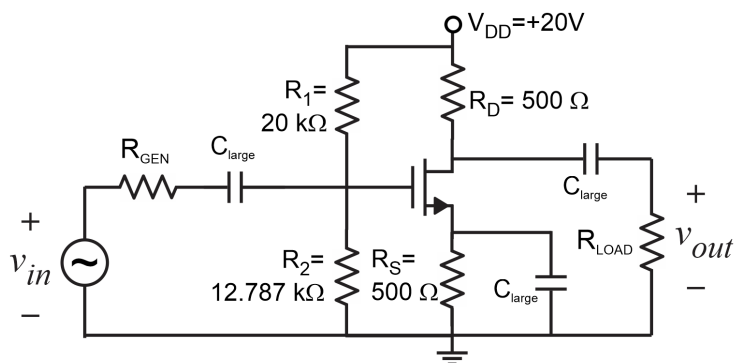B) Common Source Amplifier with bypassed source resistorC) Common Drain (a.k.a. Source Follower)D) Common Source Amplifier with bypassed source resistor

## 2) Hand Calculation of Harmonic Distortion

Background: When the input signal to a non-linear network is a sinusoid ( $\cos\omega t$ ) at frequency  $\omega$  ( $=2\pi f$ ). The output from this network may contain a DC term, a fundamental frequency ( $\omega$ ), and a set of harmonics ( $2\omega, 3\omega, 4\omega, \dots$ ).

$$\text{Input} = \cos\omega t$$

$$\text{Output} = \text{DC} + A\cos\omega t + B\cos2\omega t + C\cos3\omega t + \dots$$

The 2<sup>nd</sup> harmonic distortion (2HD) at the output is defined as the ratio of the amplitude in the 2<sup>nd</sup> harmonic to the amplitude of the fundamental, namely

$$2HD (\%) = B/A \times 100\%$$

### Questions:

- A) Find an expression for the 2<sup>nd</sup> harmonic distortion (2HD) for an n-channel MOSFET using the following expression for saturated drain current,  $i_D$ . The 2HD will be given in terms of  $A$ ,  $V_{GS}$  and  $V_{TN}$ .

Assume a sinusoidal gate-source voltage,  $v_{gs} = A\cos\omega t$

$$\text{Hint: } \cos^2\theta = \frac{1}{2} + \frac{1}{2}\cos2\theta$$


$$i_D = \frac{k_N}{2}(V_{GS} - V_{TN})^2 + k_N(V_{GS} - V_{TN})v_{gs} + \frac{k_N}{2}v_{gs}^2$$

- B) What is the value of  $A$  (amplitude of  $v_{gs} = A\cos\omega t$ ) that produces a 1% 2HD?

Assume that  $V_{GS} = 2.8\text{V}$  and  $V_{TN} = 2.6\text{V}$ .  $V_{GSQ} - V_{TN}$

①

②  $V_{TN} = 2.6V$ ,  $k_n = 0.06 A/V$

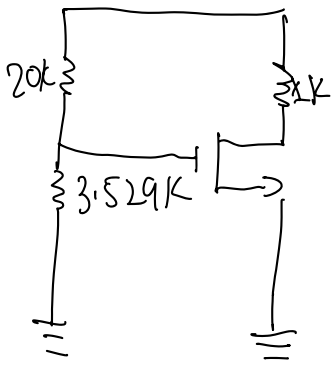

$V_{DS} = 10.4$

$V_{GS} = 3.0$

$I_{DQ} = 9.6mA$  It's in saturation.


$g_m = \frac{2I_{DQ}}{2V_{GS}}$

$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$

$= 2k_n (V_{GS} - V_T)$

$= 2(0.06)(3 - 2.6) = 0.048 A/V$

### AC Analysis

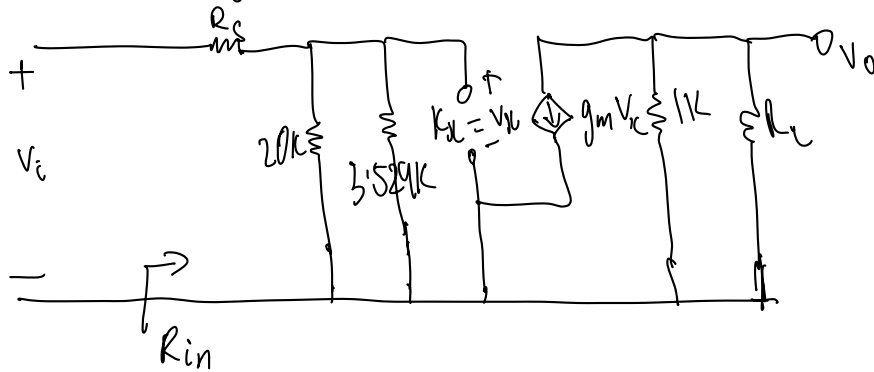

$\frac{V_{out}}{V_{in}} = \frac{V_o}{V_x} = \frac{-g_m V_x (1k)}{V_x}$


$= -g_m (1k)$   
 $= -0.048 (1k)$   
 $= -48$

$R_{in} = (20k || 3.529k) + R_s = 3k + R_s$

$R_{out} = 1k || R_L$

③  $g_m = 0.048 A/V$  for this circuit

### AC Analysis

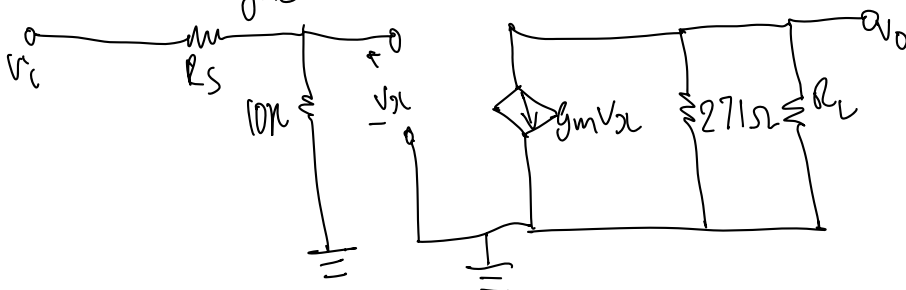


$\frac{V_{out}}{V_{in}} = -g_m (271\Omega) = -13.008$

$R_{in} = 10k + R_s$

$R_{out} = 271\Omega || R_L$

⑦  $g_m = 0.048 \text{ A/V}$

Ac Analysis

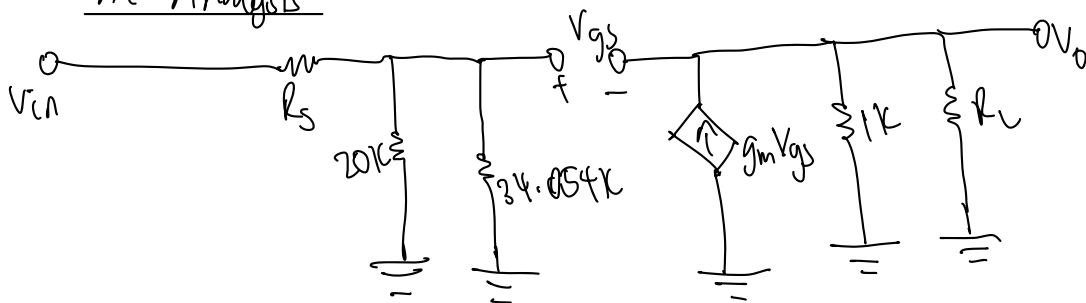

$$\frac{V_o}{v_{in}} = \frac{g_m V_{gs}(1k)}{V_{gs} + g_m V_{gs}(1k)} = g_m(1k)$$

$$= \frac{0.048(1k)}{1 + 0.048(1k)} = \frac{48}{49} \approx 0.979$$



$$R_{in} = (20 \parallel 34.05k) + R_s = 12.64R_s$$

$$R_{out} = 1k \parallel R_L$$

⑧  $V_{in} = 2.6V$ ,  $k_n = 0.06 \text{ A/V}^2$ ,  $V_{GS} = 3V$

$$I_{DQ} = 9.6 \text{ mA}, V_{DS} = 10.4V$$
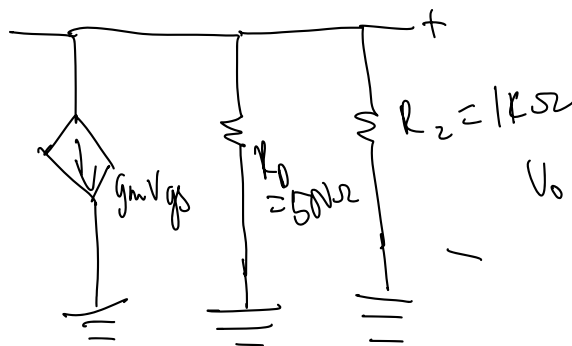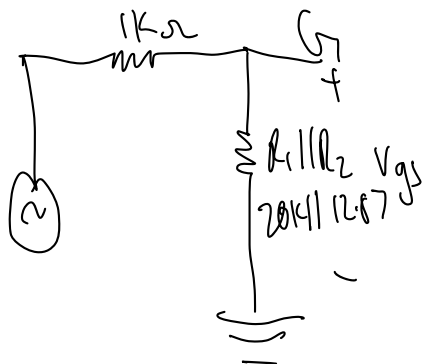
$$g_m = \frac{I_{DQ}}{V_{GS}} = \frac{9.6}{3} = 3.2 \text{ mA/V}$$



$$V_o = -g_m V_{gs}(R_D \parallel R_L)$$

$$= -3.2(1k \parallel 0.5) V_{gs} = -1.0656 V_{gs}$$

$$V_{gs} = \frac{V_{in}(R_1 \parallel R_2)}{R_1 \parallel R_2 + R_{sig}} = \frac{V_{in}(9.83k)}{8.83k} = V_{in}(0.886)$$

$$V_o = -1.0656(0.886)V_{in}$$

$$A = \frac{V_o}{v_{in}} = -1.022 \quad \left| \begin{array}{l} R_i = R_1 \parallel R_2 = 7.83k\Omega \\ R_o = R_D = 0.5k\Omega = 500\Omega \end{array} \right.$$

②

$$i_D = K_n (V_{gsQ} - V_{TN})^2 + 2K_n (V_{gsQ} - V_{TN}) A \cos(\omega t) + K_n A^2 \cos^2(\omega t)$$

$$K_n A^2 \cos^2(\omega t) = K_n A^2 \left( \frac{1}{2} + \frac{1}{2} \cos(2\omega t) \right)$$

$\Rightarrow$  Amplitude of 1st harmonic is  $(V_{gsQ} - V_{TN})A$

$\Rightarrow$  Amplitude of 2nd harmonic is  $K_n A^2 / 2$

$$2HD = \frac{K_n A^2 / 2}{2A K_n (V_{gsQ} - V_{TN})} = \frac{A}{4(V_{gsQ} - V_{TN})}$$

$$\textcircled{b} \quad V_{gsQ} = 2.8V, \quad V_{TN} = 2.0V$$

$$2HD = \frac{A}{4(2.8 - 2.0)} = \frac{A}{0.8} = \frac{1}{100} \Rightarrow A = 8mV$$

So we got that the incremental voltage  $v_{gs}$ , that rides on top of quiescent voltage  $V_{gsQ}$ , need to have a amplitude less than 8mV, for the given  $V_{gsQ}$  and  $V_{TN}$ , to have 2HD less than 1%.