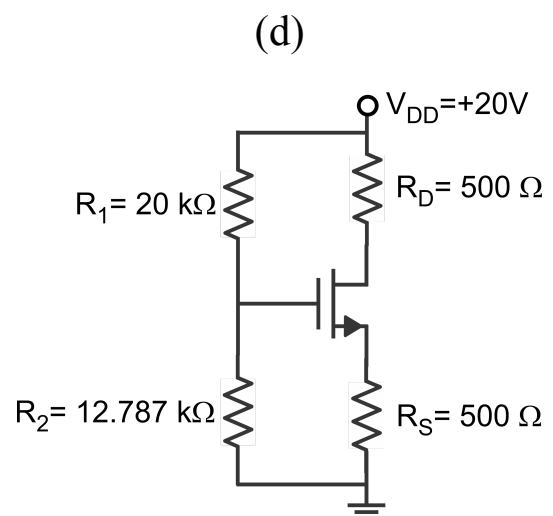
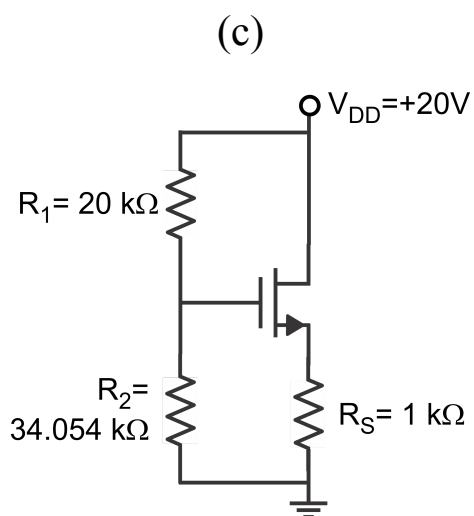
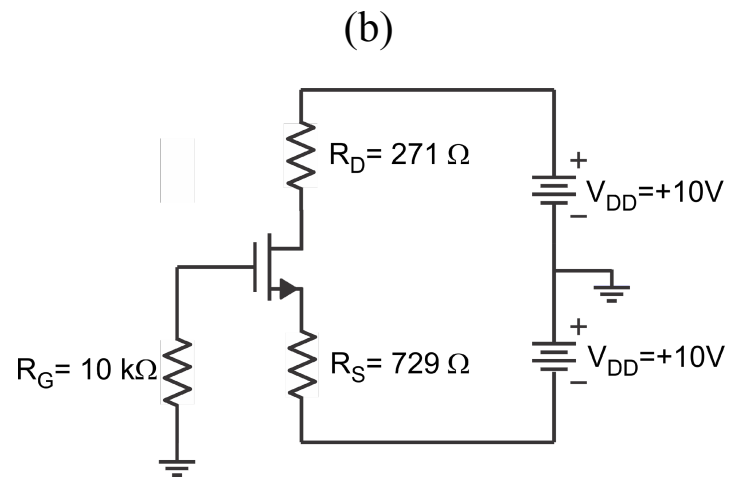
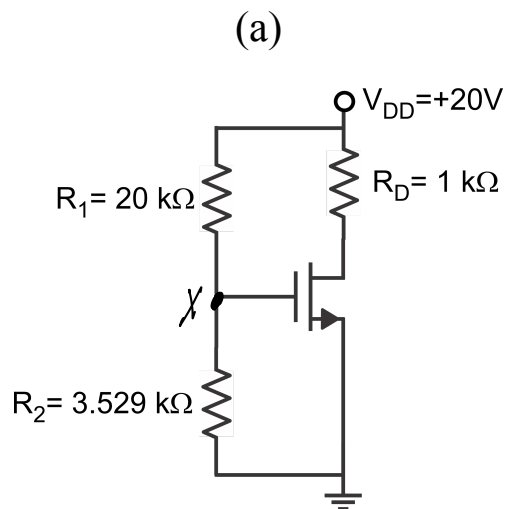


- 1) For the following four FET circuits, the FET parameters are  $V_{TN} = 2.6V$  and  $k_N = 0.12 A/V^2$ . For each circuit, the bias point (Q-point) is the same. You may use an online calculator to solve any quadratic equations.

Find for  $V_{GS}$ ,  $V_{DS}$ ,  $I_D$ . In all cases, verify that the transistor is “on” and operating in a saturated region.



①

a)  $V_{DD} = 20V$

$$V_{gs} = \frac{3.529 \times 20}{3.529 + 20} = 2.9997V$$

Assume mosfet is in saturation mode:

$$I_D = \frac{1}{2} K_n [V_{gs} - V_t]^2 = \frac{1}{2} \times 0.12 [2.9997 - 2.6]^2 = 9.58 \mu A$$

$$-V_{DD} + I_D R_D + V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_D R_D = 20 - 9.58 \times 1 = 10.42V$$

$$V_{DS} \geq V_{gs} - V_t$$

$$10.42 \geq 2.9997 - 2.6 \quad \boxed{\checkmark} \text{ True}$$

b)  $V_{DD} = 10V$

$$\cancel{I_{D1}} + V_{gs} + 15729 - V_{DD} = 0$$

$$I_D = \frac{10 - V_{gs}}{729}$$

Assume mosfet in saturation

$$I_D = \frac{1}{2} K_n [V_{gs} - V_t]^2$$

$$\frac{I_D - V_{gs}}{729} = \frac{1}{2} \times 0.5 [V_{gs} - 2.6]^2$$

$$\frac{10 - V_{gs}}{729} = 0.06 [V_{gs}^2 + 6.76 + 5.2 V_{gs}]$$

$$10 - V_{gs} = 43.74 V_{gs}^2 + 295.68 - 227.45 V_{gs}$$

$$43.74 V_{gs}^2 - 226.45 V_{gs} + 285.68 = 0$$

$$V_{gs} = 3 \quad \checkmark$$

$$V_{gs} = 2.171$$

$$I_D = \frac{10^{-3}}{729} = 9.6 \mu A$$

KVL:

$$-V_{DD} + I_D \cdot 271 + V_D = 0$$

$$V_D = 10 - 271 \times 9.6$$

$$= 7.39$$

$$V_{DS} = V_D - V_S = 7.39 - (-3) = 10.39 V$$

$$V_{DS} \geq V_{GS} - V_t$$

$$10.39 \geq 3 - 2.6 \quad \checkmark \text{ true}$$

$$\textcircled{C} \quad V_g = \frac{34.054}{34.054 + 20} \times 20 = 12.59 V$$

$$-V_g + V_{GS} + I_D R_S = 0$$

$$-12.59 + V_{GS} + I_D R_S = 0$$

$$I_D = \frac{12.59 - V_{GS}}{1k}$$

Assume saturation

$$I_D = \frac{1}{2} k_n [V_{GS} - V_t]^2$$

$$\frac{12.59 - V_{GS}}{1k} = \frac{1}{2} \times 0.12 [V_{GS}^2 + 6.76 - 5.2 V_{GS}]$$

$$12.59 - V_{GS} = 60 V_{GS}^2 - 312 V_{GS} + 405.6$$

$$60 V_{GS}^2 - 311 V_{GS} + 393.01 = 0$$

$$V_{GS} = 2.99 V$$

$$V_{GS} = 2.18 V$$

$$V_{GS} > V_t$$

$$I_D = \frac{12.59 - 2.99}{1} = 9.6 \mu A$$

$$-V_S + I_D R_S = 0 \Rightarrow V_S = 9.6 \mu A \times 1k = 9.6 V$$

$$V_{DS} = V_D - V_S = 20 - 9.6 = 10.4V$$

$$V_{DS} \geq V_{GS} - V_t$$

$$10.4 \geq 2.99 - 2.6 \quad \checkmark \text{ true}$$

$$d) V_g = \frac{12.787}{12.787 + 20} \times 20 = 7.8V$$

KVL:

$$-V_g + V_{GS} + I_D 500 = 0$$

$$I_D = \frac{7.8 - V_{GS}}{500}$$

Assume saturation:

$$I_D = \frac{1}{2} k_n [V_{GS} - V_t]^2$$

$$\frac{7.8 - V_{GS}}{500} = \frac{1}{2} \times 0.12 [V_{GS} - 2.6]^2$$

$$7.8 - V_{GS} = 80 V_{GS}^2 + 202.8 - 156 V_{GS}$$

$$V_{GS} = 3 \quad \checkmark \quad V_{GS} = 2.16$$

$$I_D = \frac{7.8 - 3}{500} = 9.6 \text{ mA} \quad \left| \begin{array}{l} -V_S + I_D R_S = 0 \\ V_S = I_D R_S = 4.8 \end{array} \right.$$

$$-V_{DD} + 500 I_D + V_{DS} = 0$$

$$V_{DS} = 20 - 500 \times 9.6 \text{ mA} = 15.2V$$

$$V_{DS} \geq V_{GS} - V_t$$

$$10.4 \geq 3 - 2.6 \quad \checkmark \text{ true}$$